 


# EL318: Lecture 3-1


## Pipelining

With thanks to Srin Devadas at MIT and his course *Computation Structures*

# *Pipelining*


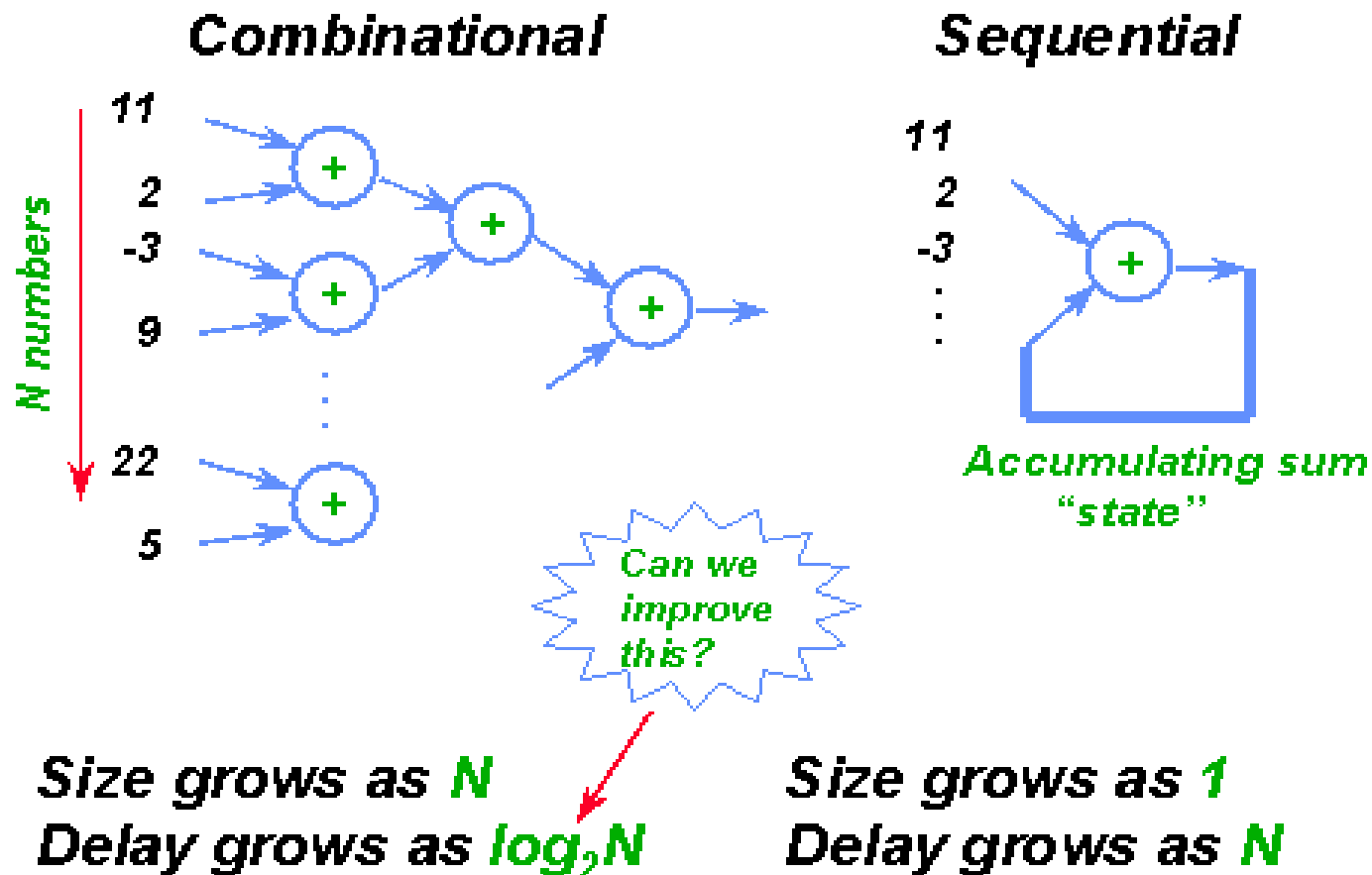
## Motivation: Adding a column of numbers



# Brent's Theorem

Let  $A$  be a given algorithm with a parallel computation time of  $t$ . Suppose that  $A$  involves a total number of  $m$  computational operations. Then  $A$  can be implemented using  $p$  processors in  $O(m/p + t)$  parallel time.

**Proof:** Let  $m(i)$  be the number of computational operations performed (in parallel) in step  $i$  of  $A$ , the algorithm provided. Using  $p$  processors this can be simulated in  $m(i)/p + 1$  time. Now summing over all  $i$ ,  $1 \leq i \leq p$ , we get the stated parallel computation time because  $m = m(1) + m(2) + \dots + m(p)$ .

## Observe... An Assembly Line




- Length **L** objects (and workers), moves at rate **R** objects/minute
- Each task should take at most \_\_\_\_\_ minutes
- An object is processed in \_\_\_\_\_ minutes
- Workers always have an object in front of them

## Definitions




- **Latency:** Time for one object to pass through the system is  $L/R$
- **Throughput:** Rate of objects going through is  $R$

## Adding Numbers: A Closer Look

 

## Combinational Throughput and Latency

 


Delay of + is  $t_{pd}$

$$\text{Latency} = 2 t_{pd}$$


$$\text{Throughput} = \frac{1}{2 t_{pd}}$$




## Pipelined Throughput and Latency

 

## Inhomogenous Pipeline

 


## ILL-Formed Pipelines

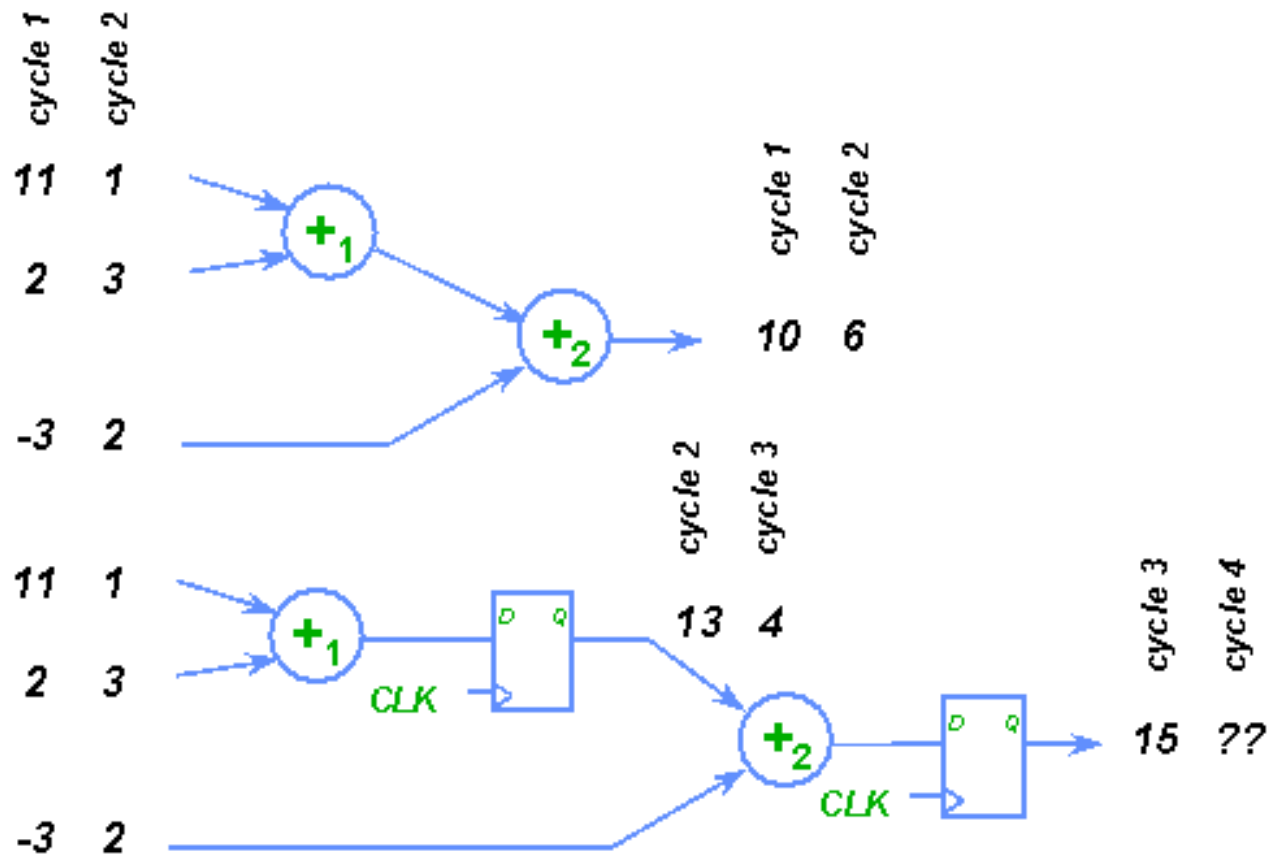

 
## Pipeline Well-Formedness

- Same number of flip-flops along any path from any input to any output
  - Insures that every computational unit sees inputs in phase


 
## ***k**-Pipelines*

- **k** flip-flops on each input-output path
- Always have flip-flops on each output



**Clock period is maximum propagation delay from flip-flop output (or circuit input) to flip-flop input**